

# **Table of Contents**

## **Part 1: Audio Power Amplifier Basics**

- 1. Introduction**
- 2. Power Amplifier Basics**
- 3. Power Amplifier Design Evolution**
- 4. Negative Feedback Compensation and Slew Rate**
- 5. Amplifier Classes, Output Stages and Efficiency**
- 6. Summary of Amplifier Design Considerations**

## **Part 2: Advanced Power Amplifier Design**

- 7. Input and VAS Circuits**
- 8. DC Servos**
- 9. Advanced Forms of Feedback Compensation**
- 10. Output Stage Design and Crossover Distortion**
- 11. MOSFET Power Amplifiers**
- 12. Error Correction**
- 13. Other Sources of Distortion**

## **Part 3: Real World Design Considerations**

- 14. Output Stage Thermal Design and Stability**
- 15. Safe Area and Short Circuit Protection**
- 16. Power Supplies and Grounding**
- 17. Clipping Control and Civilized Amplifier Behavior**

**18. Interfacing the Real World**

## **Part 4: Simulation and Measurement**

**19. SPICE Simulation**

**20. SPICE Models and Libraries**

**21. Audio Instrumentation**

**22. Distortion and its Measurement**

**23. Other Amplifier Tests**

## **Part 5: Topics in Amplifier Design**

**24. The Negative Feedback Controversy**

**25. Amplifiers without Negative Feedback**

**26. Balanced and Bridged Amplifiers**

**27. Integrated Circuit Power Amplifiers and Drivers**

## **Part 6: Class D Audio Amplifiers**

**28. Class D Audio Amplifiers**

**29. Class D Design Issues**

**30. Alternative Class D Modulators**

**31. Class D Measurement, Performance and Efficiency**